
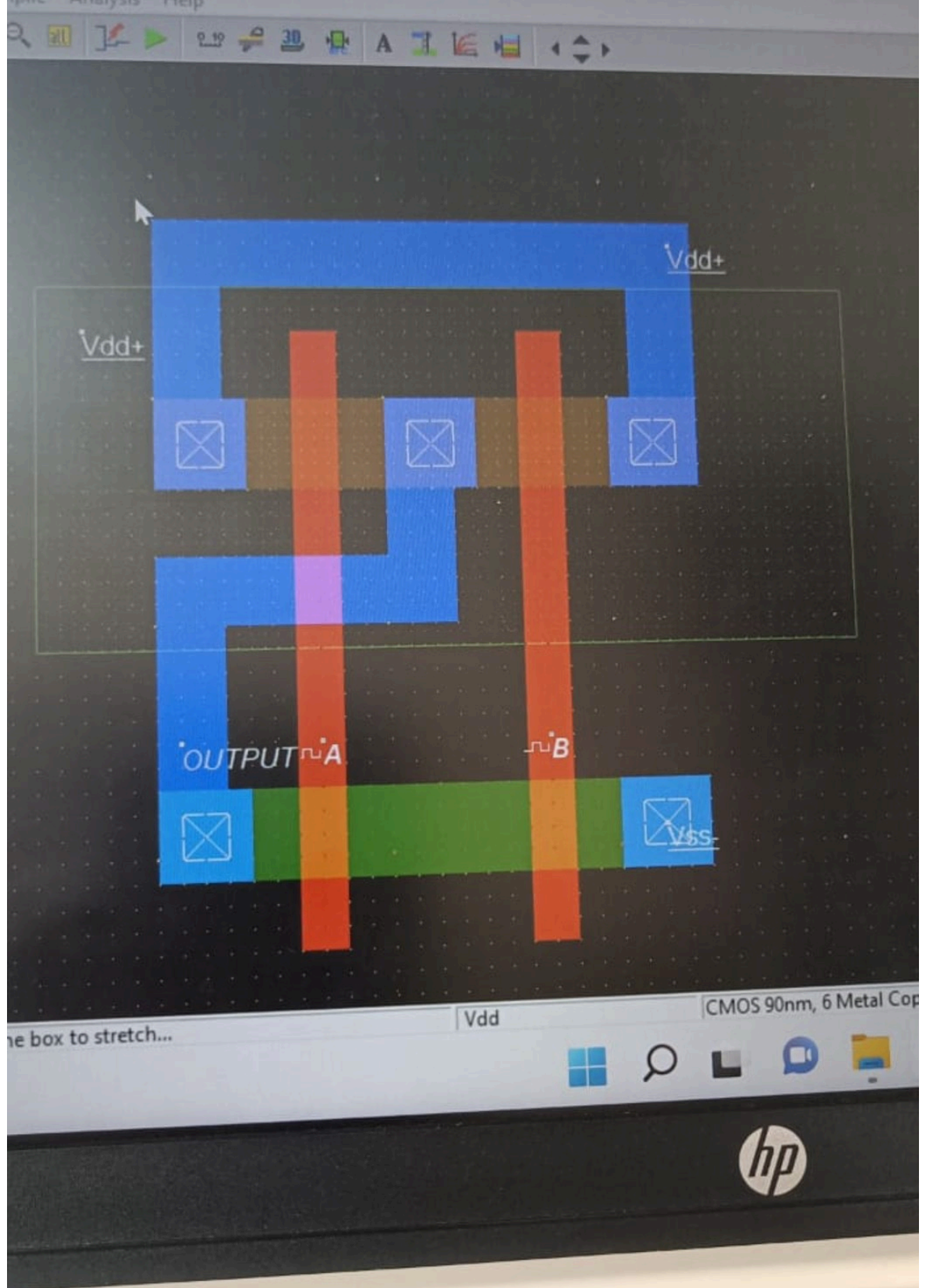


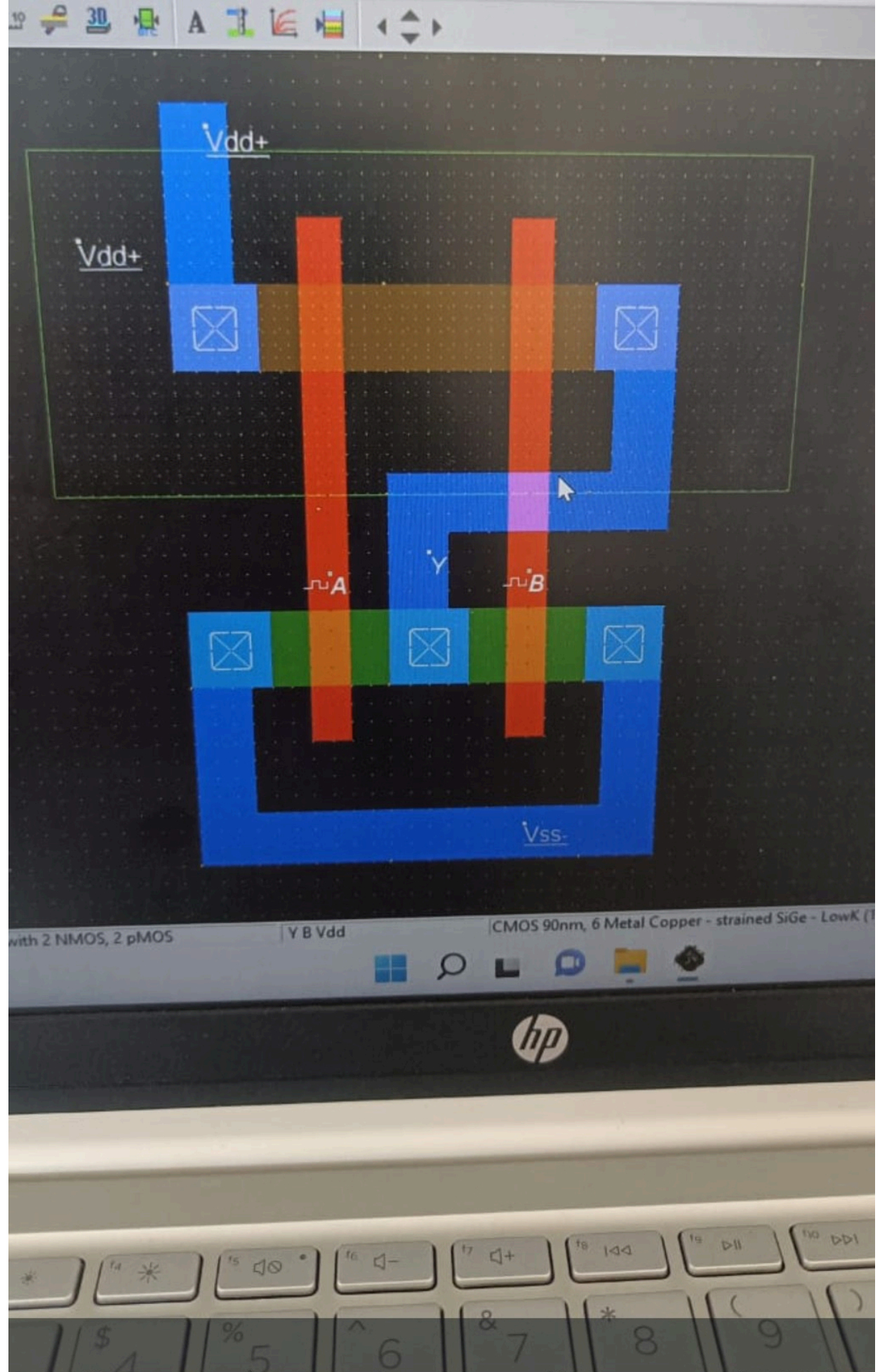
Pmos ani Nmos red join kla blue join
kla Dig of INVERTER



NAND gate p diffusion n diffusion of 24×4
 and gap of 12 place 3 p+diffusion and 2
 n+diffusion nwell of 36×16




Same rule as abovediagram of NOR

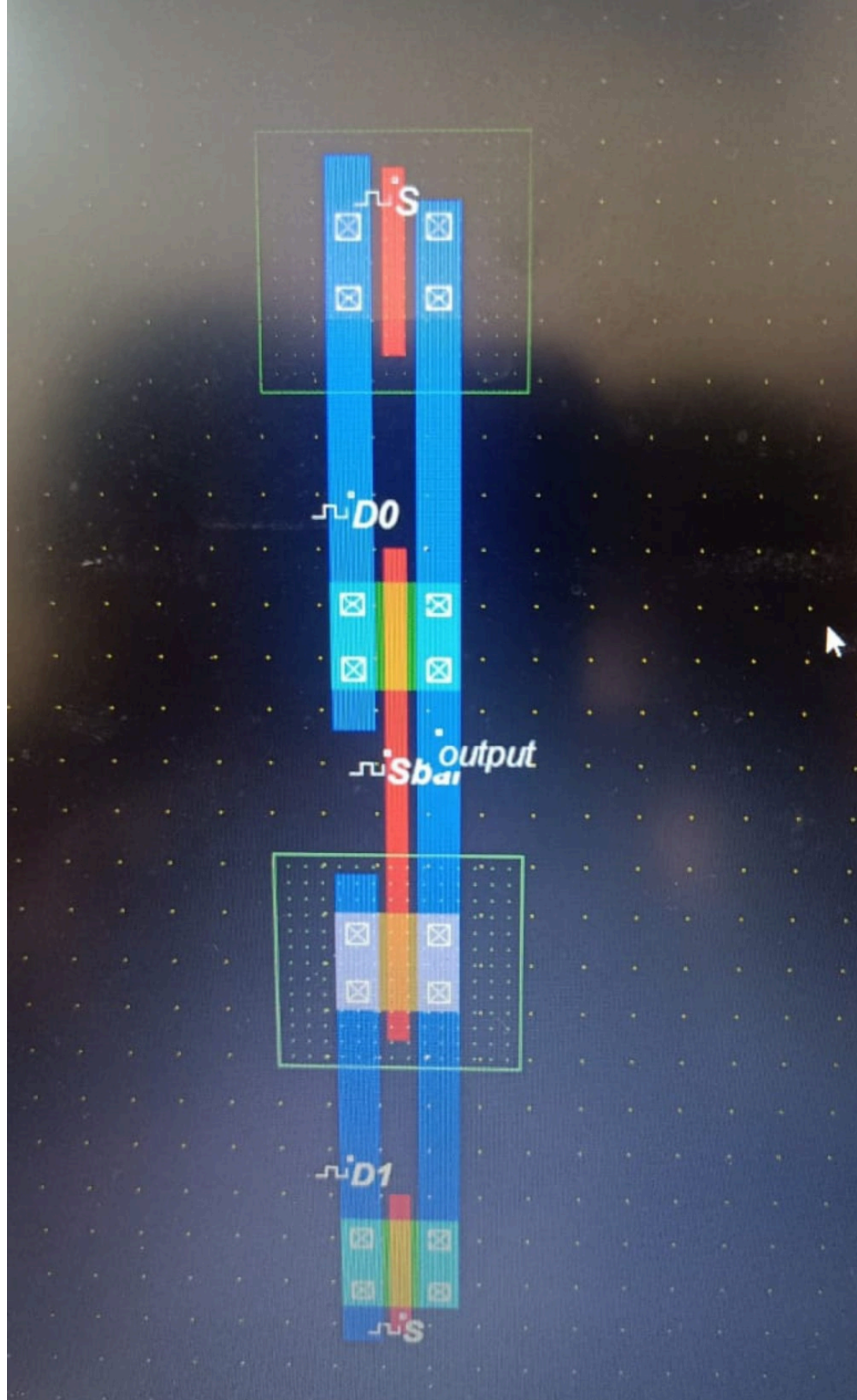

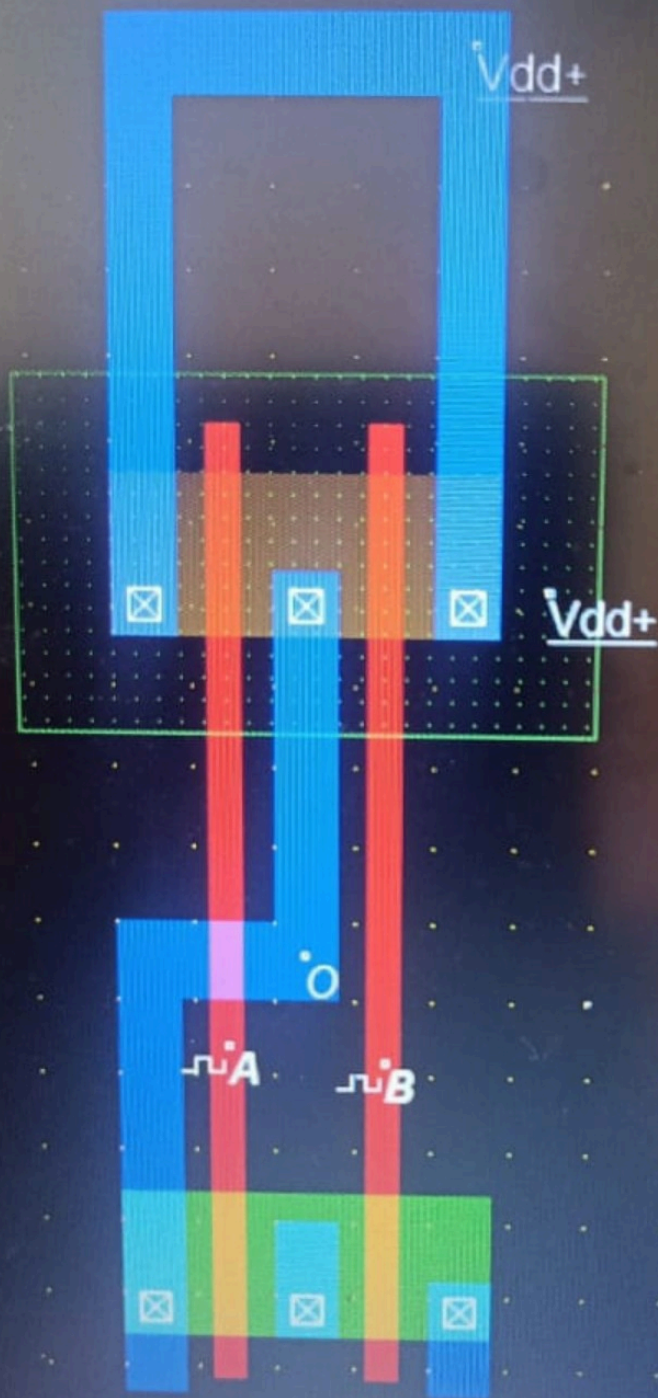P N P N Alternate ghya varche 2 connect metal ny ...khalche 2 connect metal ny and middle Wale gate connect kra ani zla





N mos and pmos are selected for 2 devices and connection is takes placed